

Example #3: Determine the unknown currents for each of the following circuits.

